

*Analysis of Electrical Noise in
Piezoelectric Sensors*

Jeffrey Dosch

Bill Hynd

PCB Piezotronics, Depew NY

IMAC XXV February 19-22, 2007

Orlando FL

What is noise?

- Noise is any undesired signal.
- Electrical noise is intrinsic to sensor.
 - Noise floor will limit ability to resolve of small signals
- Extrinsic noise. Noise induced because of sensor susceptibility to environment.
 - Thermal transients
 - Base strain
 - Cable strain
 - Magnetic fields
 - Electric fields
 - EMI
 - Cross axis motion
 - Ground loops
 - Channel cross talk
 - Cable triboelectric
 - etc

Outline


- How noise is measured and specified.
- Basic construction of piezoelectric sensors.
- Noise considerations in sensor design.
 - Thermal noise (Resistor)
 - FET noise
 - Internal amplifiers (ICP®)
 - Voltage amplifiers.
 - Charge amplifiers.
 - External charge amplifiers.

Noise measurement

- Noise is a random process.
 - Time domain noise specified by the rms value.
 - Volts rms; g rms; m/s² rms
 - In frequency domain noise is specified by power spectral density.
 - V²/Hz; V/√Hz; g²/Hz; g/√Hz


PEAK VALUE

| | |
|-----|---------------|
| <1σ | 68.2% of time |
| <2σ | 95.4% of time |
| <3σ | 99.7% of time |

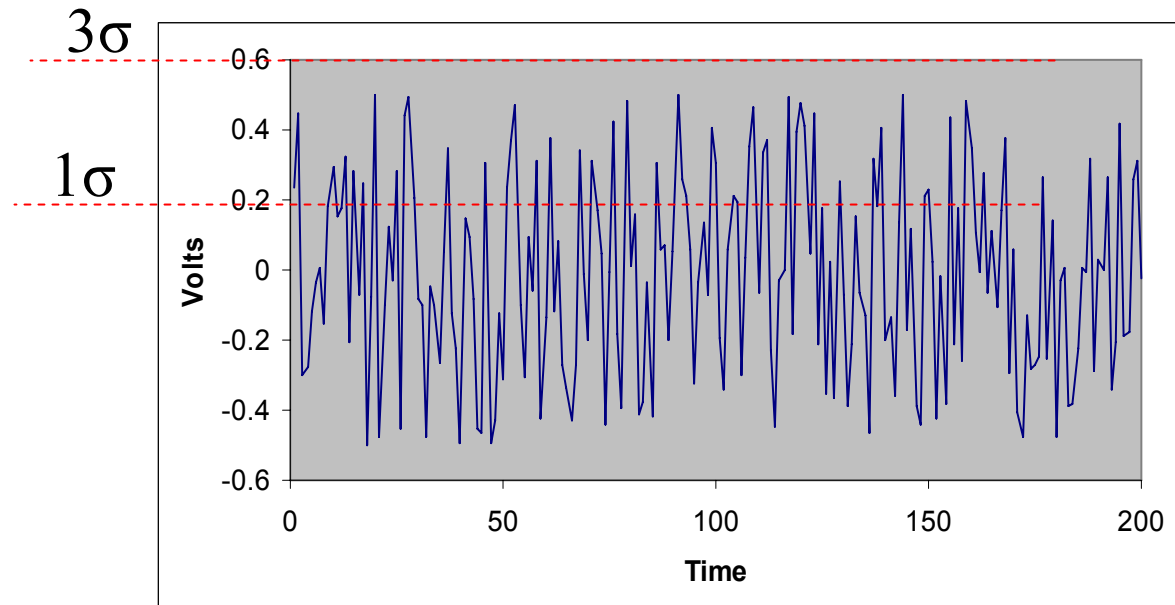




Noise measurement

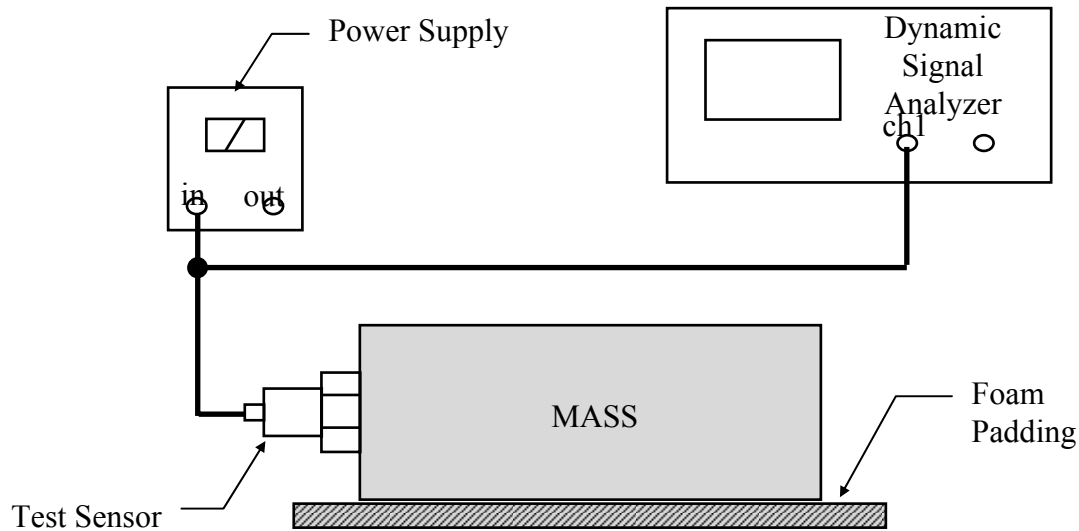- Mount SUT in quiet environment.
- Spectrum Analyzer to Measure PSD




Noise measurement

- RMS noise found by integrating PSD.

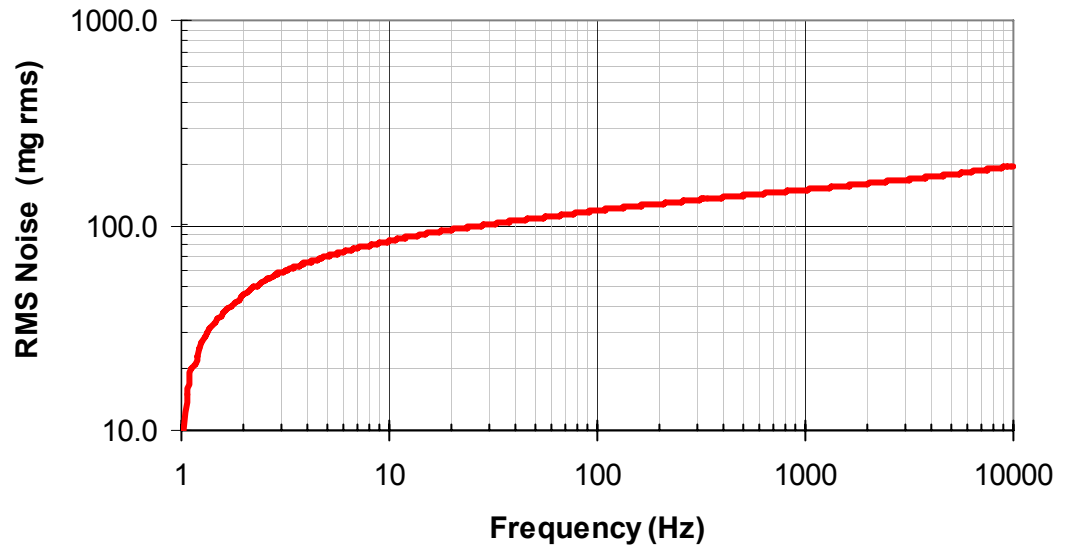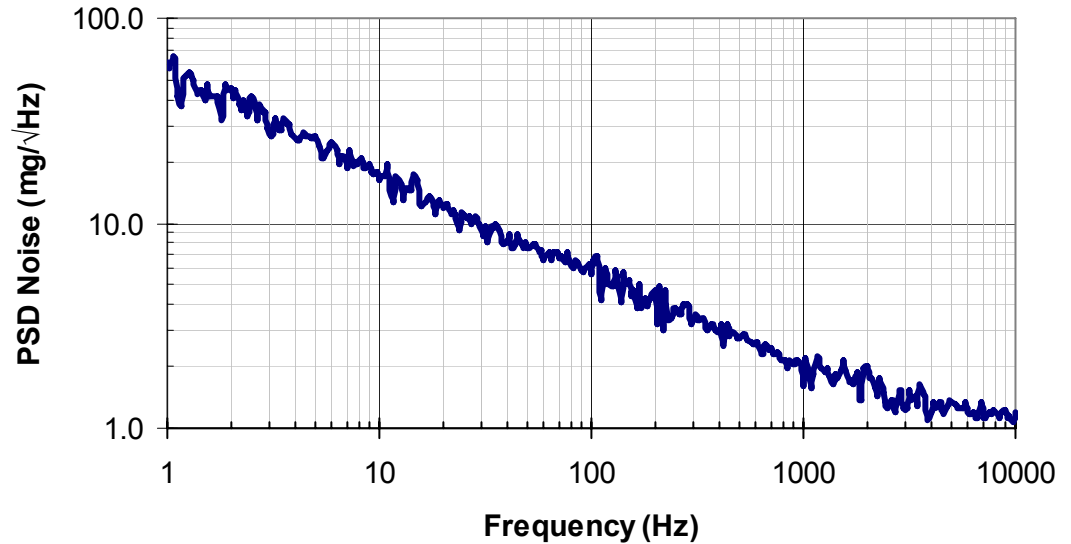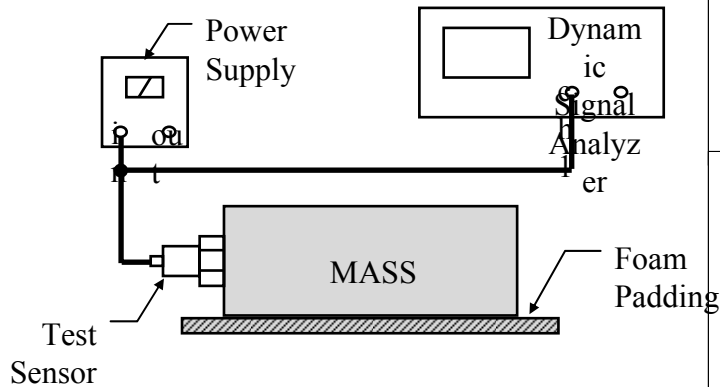

Accelerometer construction

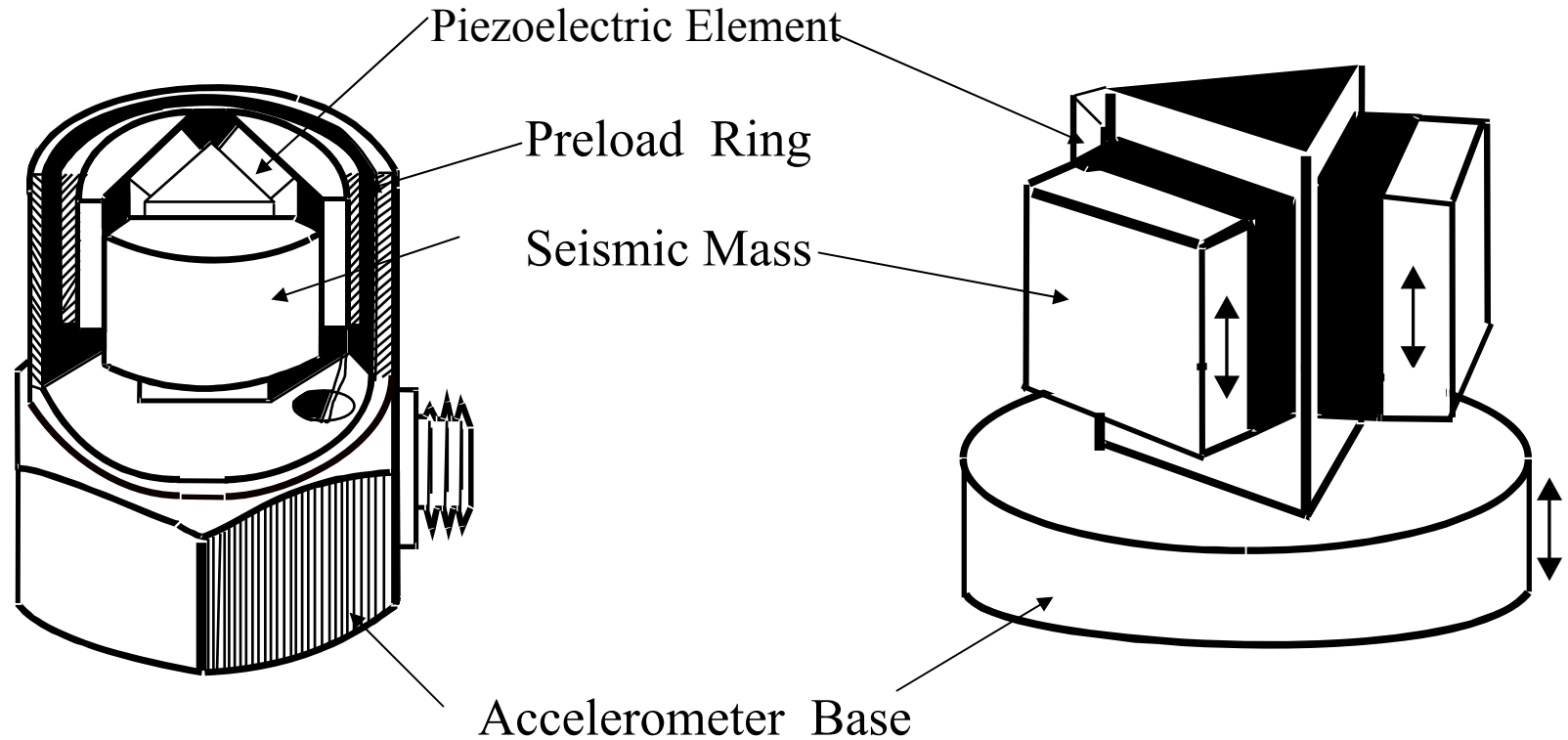



Piezoelectric materials

- PZT piezoceramic
 - High charge sensitivity
 - $d_{15} = 580 \text{ pC/N}$ (charge constant)
 - $g_{15} = 38 \text{ V-m/N}$ (voltage constant)
- Quartz
 - Stable, not pyroelectric
 - Low charge sensitivity, but high voltage sensitivity
 - $d_{26} = 4.6 \text{ pC/N}$ (charge constant)
 - $g_{26} = 118 \text{ V-m/N}$ (voltage constant)

Time constant


- Piezo modeled as capacitor and voltage source.
- Resistor creates RC filter to attenuate thermal response.
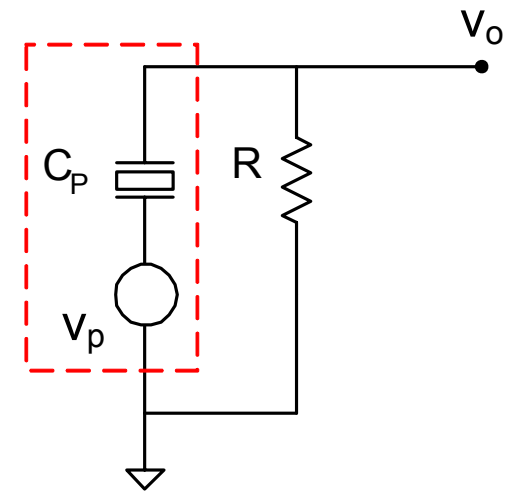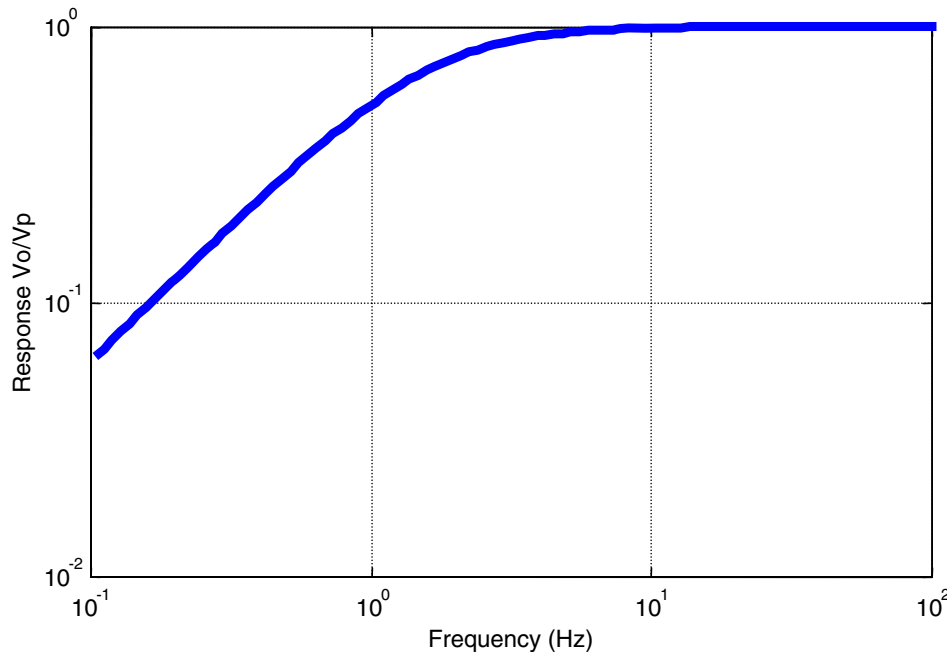
$$\frac{V_o}{V_p} = \frac{RCs}{1 + RCs} = \frac{\tau s}{1 + \tau s}$$




Voltage amplifier

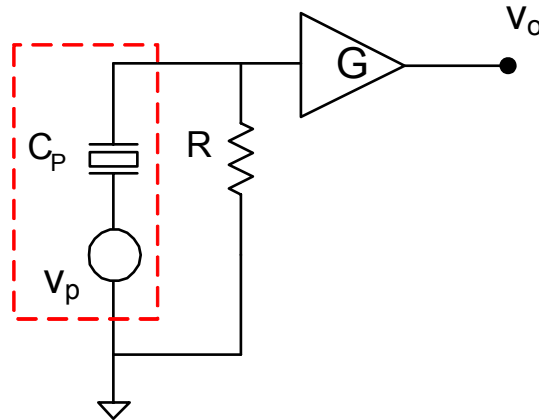- Amplifies and buffers piezo element voltage.
- Used with quartz sensors.
- Noise from two sources (RSS addition):
 - Resistor (Thermal noise)
 - Amplifier
 - MOSFET transistor



Thermal noise

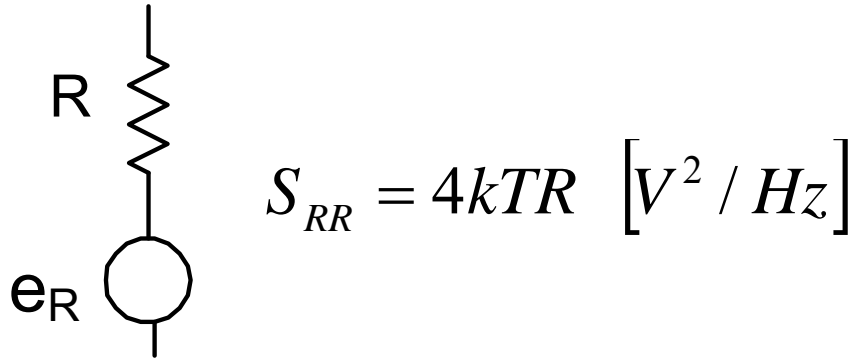- Modeled as voltage in series with the resistor.



- Thermal noise is in proportion to temperature and resistor value.
 - At RT: $R=1e9$, $e_R = 4 \mu V / \sqrt{Hz}$; $R=1e12$, $e_R = 0.12 mV / \sqrt{Hz}$
- Low noise circuits utilize resistors with low excess noise.
 - Excess noise is noise greater than theoretical
 - Excess noise has $1/f$ spectrum. Is proportional to DC current flow.



Thermal noise: output referred

- Transfer function for thermal noise

$$H_R(s) = \frac{V_o}{V_R} = \frac{G}{1 + RC_p s}$$

- Spectral density

$$S_{oo}(\omega) = S_{RR} |H_R|^2 = \frac{4kTRG^2}{1 + (RC_p)^2 \omega^2} = \frac{4kTG^2(\tau / C)}{1 + (\tau)^2 \omega^2}$$

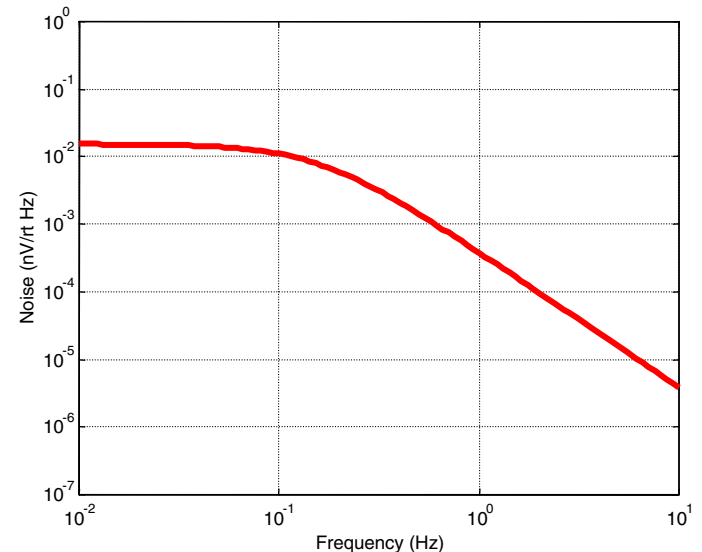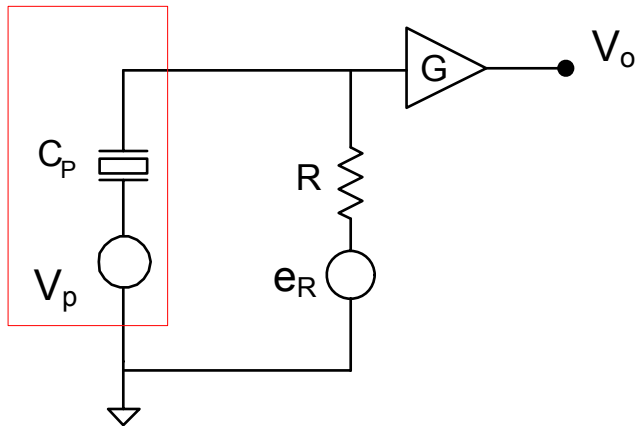


Thermal noise: time constant

- Longer time constant, lower noise

$$\omega \gg 1 / \tau$$
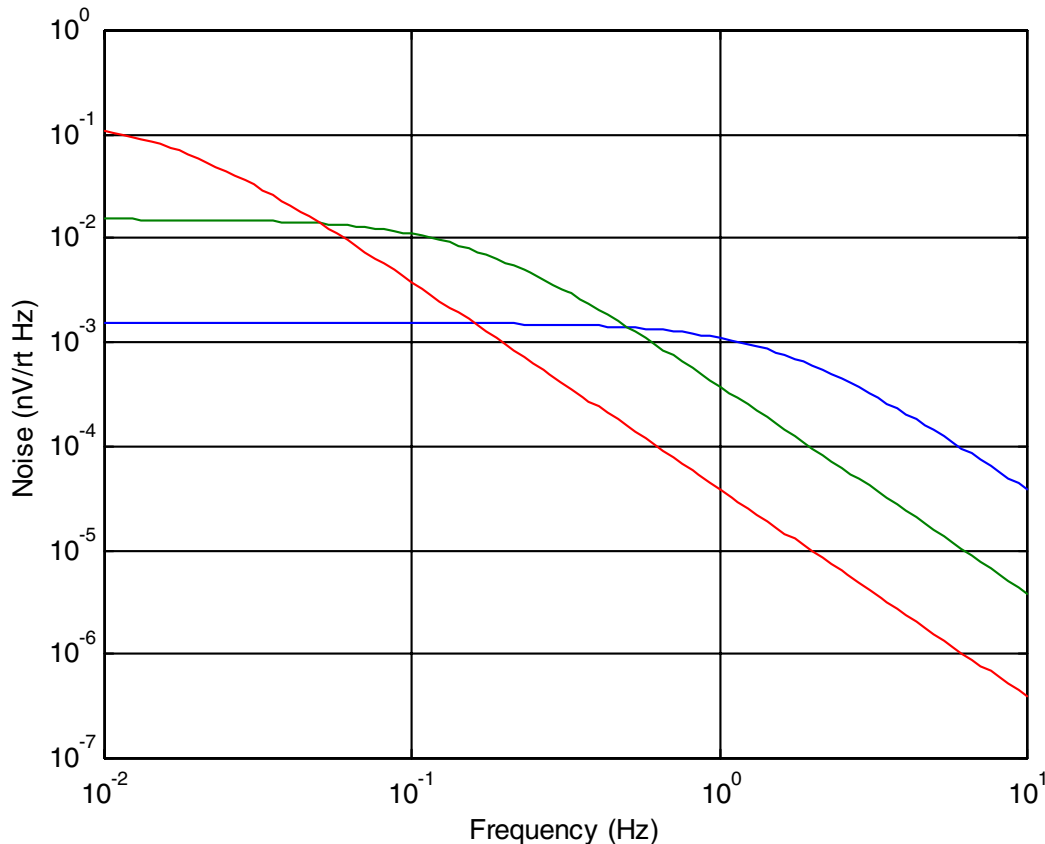
$$S_{oo}^{1/2}(\omega) = \sqrt{4kT} g \frac{1}{\omega \sqrt{\tau C}}$$



$$\tau = .1$$

$$\tau = 1$$


$$\tau = 10$$

Thermal noise RMS

- RMS found by integrating spectral noise:



$$e_n^2 = \int_0^\infty S_{rr} |H_R|^2 d\omega = kT \frac{1}{C} \quad e_n = \sqrt{kT} \frac{1}{\sqrt{C}}$$

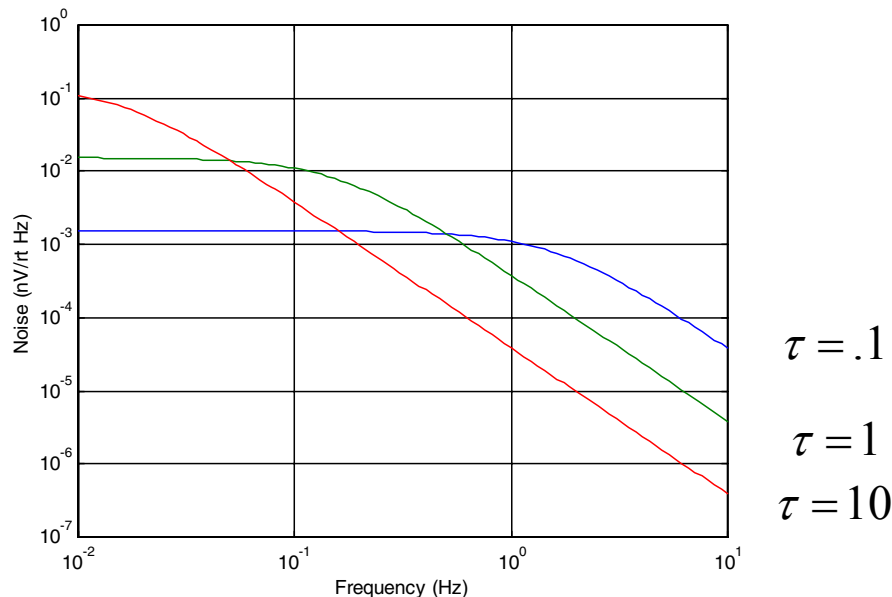- RMS noise depends only on capacitance!
 - Real sensors have finite bandwidth.



Voltage amp noise

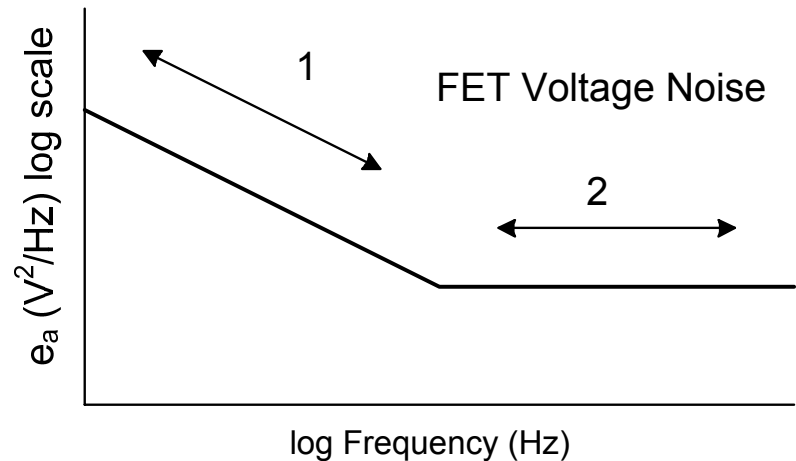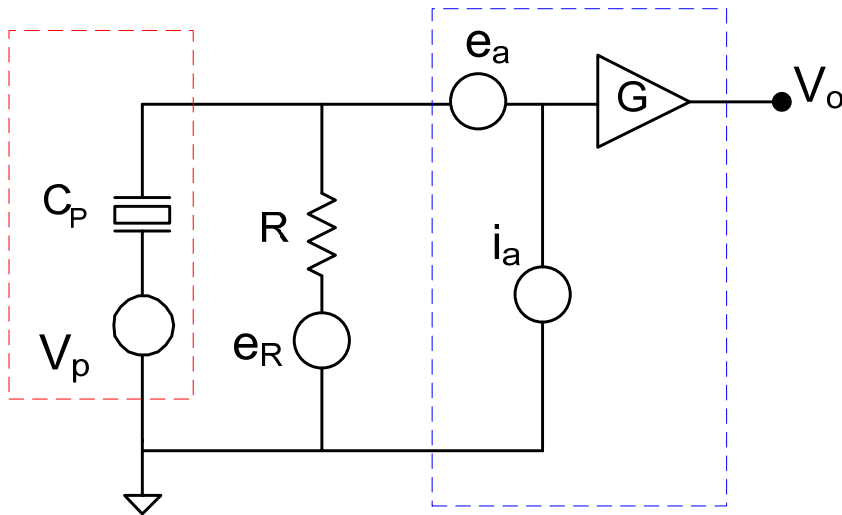- Model includes MOSFET voltage and current noise.
 - Current noise is small and can generally be ignored
 - FET voltage noise can be measured, or found from specs
 - FET noise is multiplied by amp gain



Voltage amp noise

- Total noise found by RSS of resistor and FET noise.


QUARTZ ACCEL

Tau = 1 sec

R = 2E11

Sens 10 mV/g


Gain = 2.1

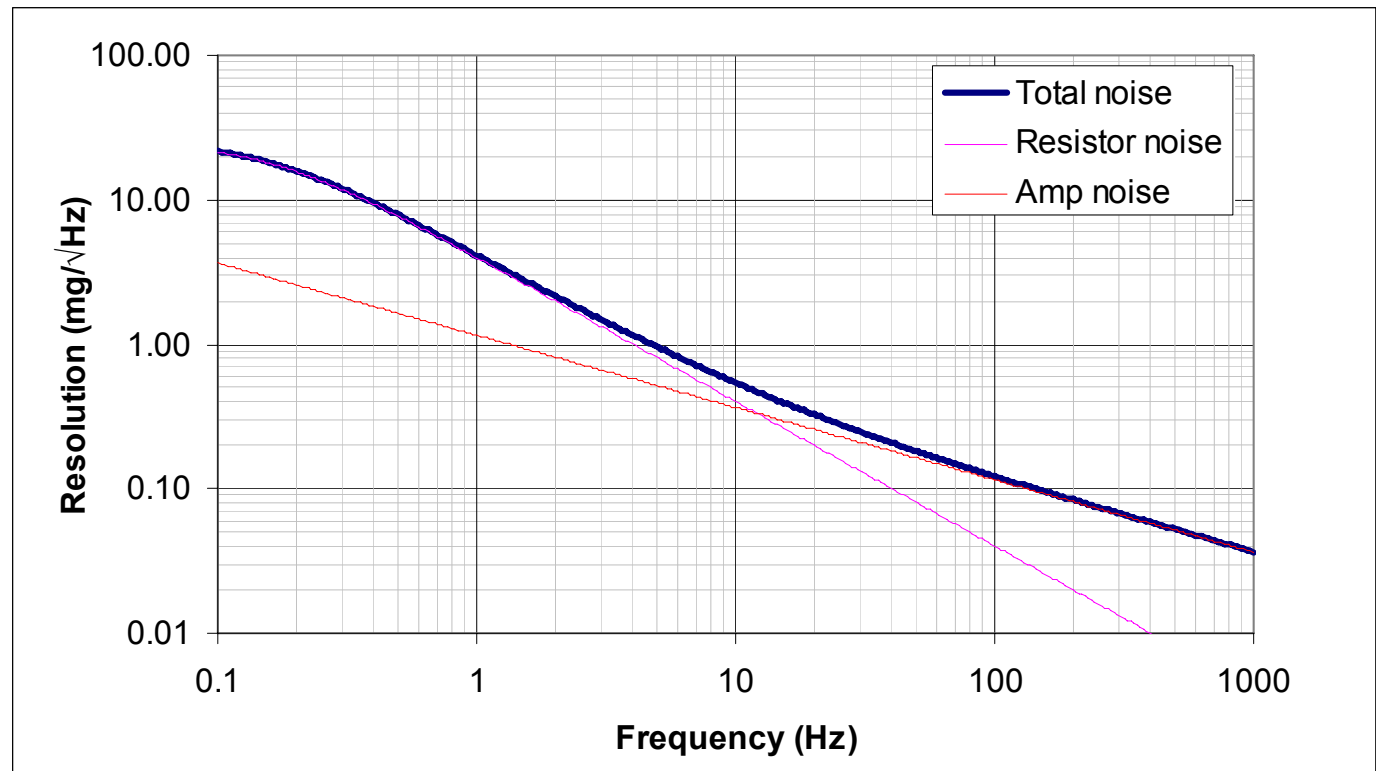

Charge amp

- Output is in proportion charge.
- Gain is:

$$G = \frac{C_p}{C} \quad V_o = GV_p$$

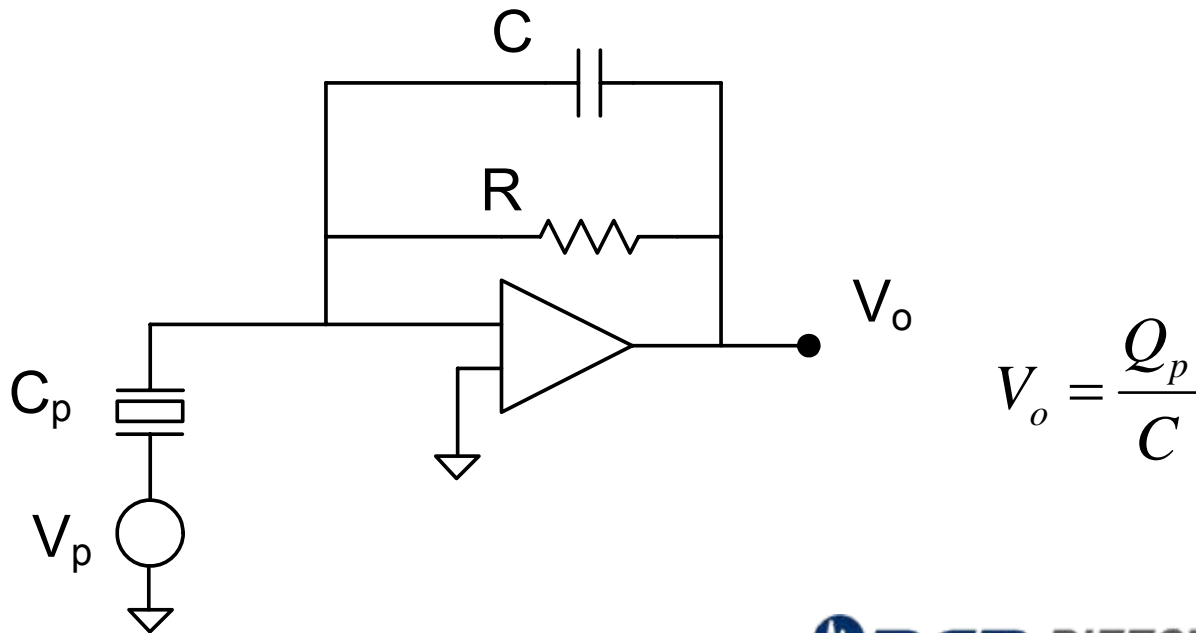



$$V_o = \frac{Q_p}{C}$$

Charge amp noise

- Thermal (resistor) noise is same as voltage amp case.
- Except, noise is independent of gain.

$$\omega \gg 1 / \tau$$
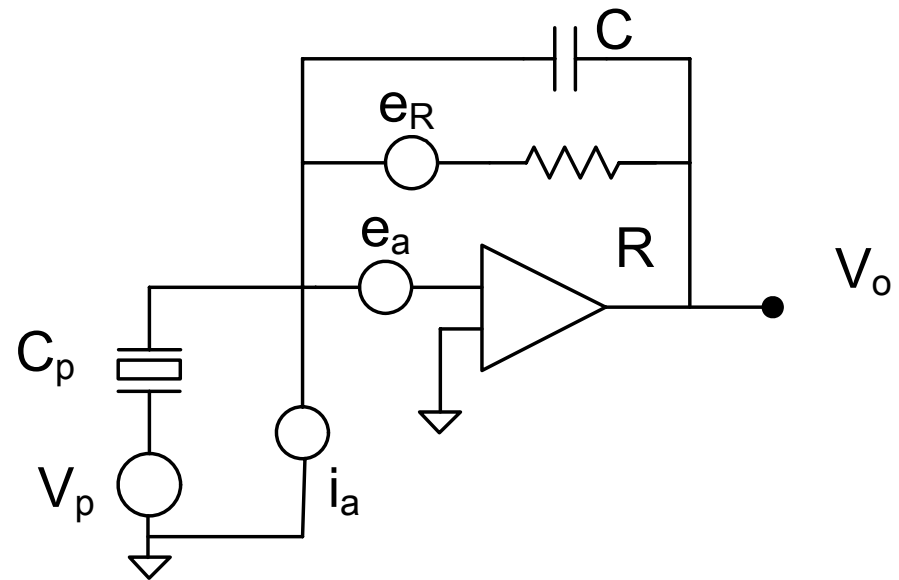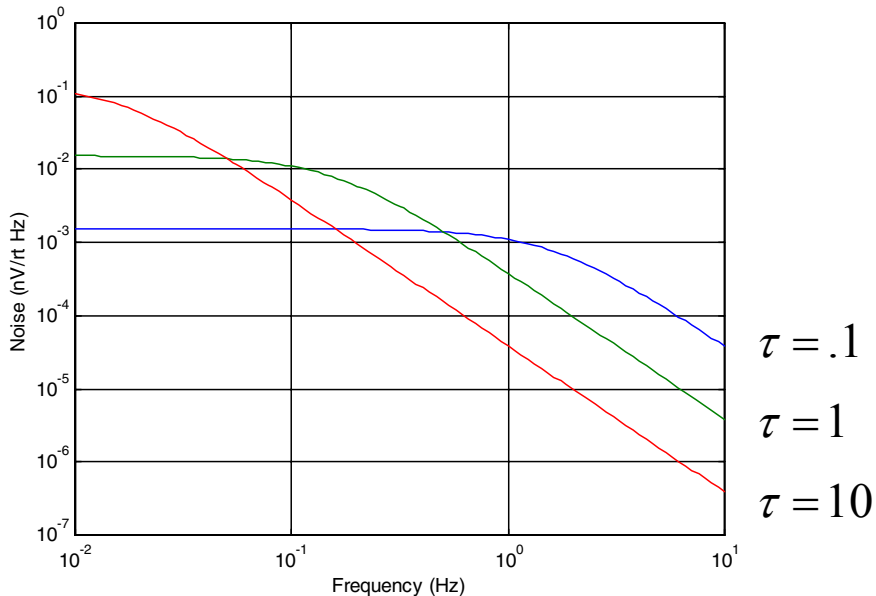
$$S_{pp}^{1/2}(\omega) = \sqrt{4kT} \frac{1}{\omega\sqrt{\tau C}}$$



Charge amp noise


- FET Current noise is usually small and can be ignored.
- FET voltage noise transfers as

$$S_{pp} = S_{aa} |H_a|^2 = \frac{V_o}{V_a} = S_{aa} \left| \frac{\tau(G+1)j\omega + 1}{1 + \tau j\omega} \right|^2 = S_{aa} \frac{\tau^2(G+1)^2\omega^2 + 1}{1 + \tau^2\omega^2}$$

- For $\omega \gg 1 / \tau$ reduces to:

$$S_{oo}^{1/2} = S_{aa}^{1/2} (G + 1)$$

$$G = \frac{C_p}{C}$$

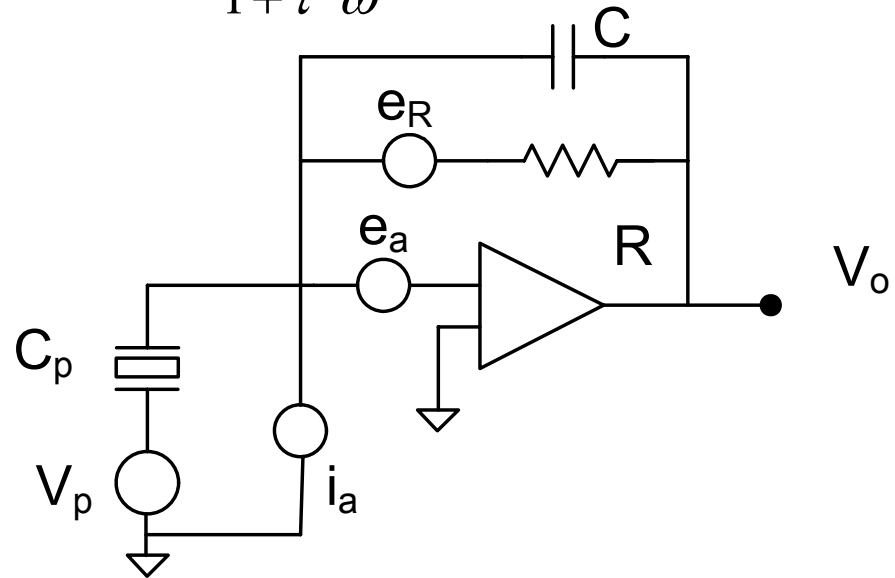


External charge amp

- Added source capacitance due to cable.
 - Amp noise gain increased

$$S_{pp}^{1/2} = S_{aa}^{1/2} (G + 1)$$


$$G = \frac{C_p + C_c}{C}$$

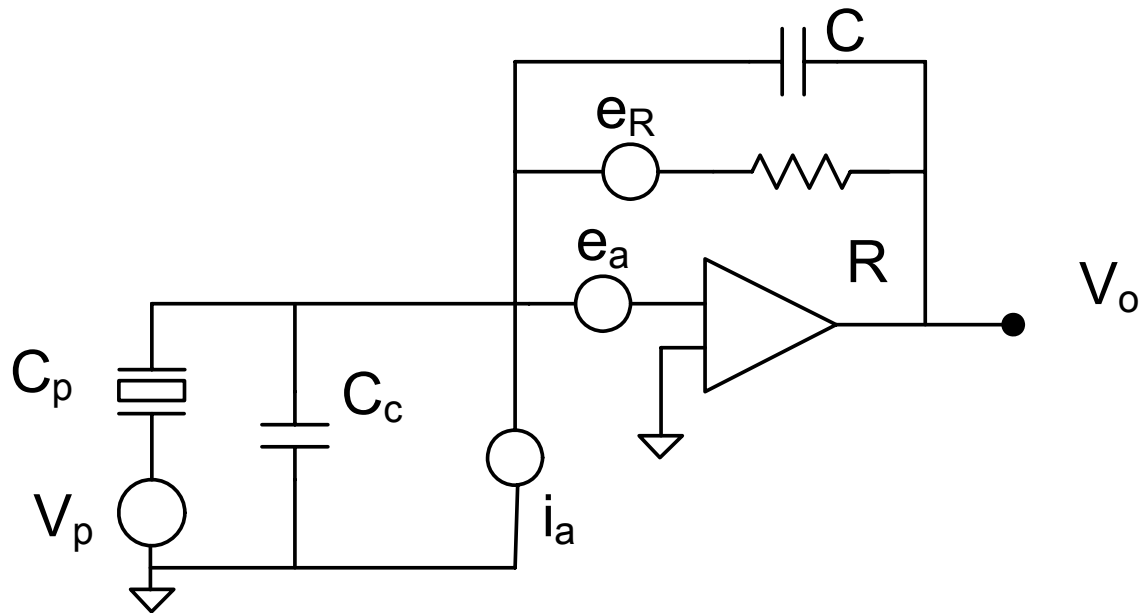

Thermal noise

- Thermal noise force in mechanical element.
- Noise force generated from damping and temperature.
- Noise is:
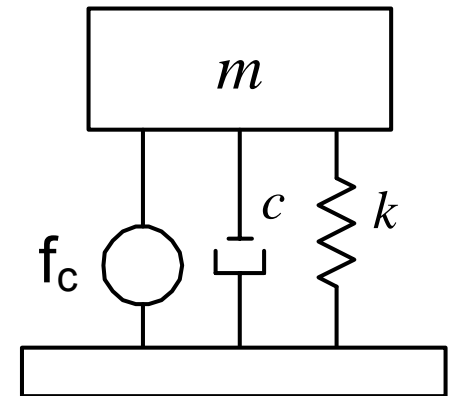
$$resolution = \sqrt{4k_B T} \sqrt{\frac{2\zeta\omega_n}{m}} \quad [\text{m/s}^2/\sqrt{\text{Hz}}]$$



- Not significant in piezoelectric sensors.
- Thermal noise is a limit to miniaturization.

Noise example: 333B30

- Design specs

$$C_p = 690 \text{ pF}$$

$$C_f = 50 \text{ pF}$$


$$\text{Amp Noise Gain} = (1 + 690/50) = 14.8$$

$$\text{Time constant} = 1\text{-}3 \text{ seconds}$$

- High gain and long time constant. Would expect that amplifier noise would dominate.

Design Example: 333B30

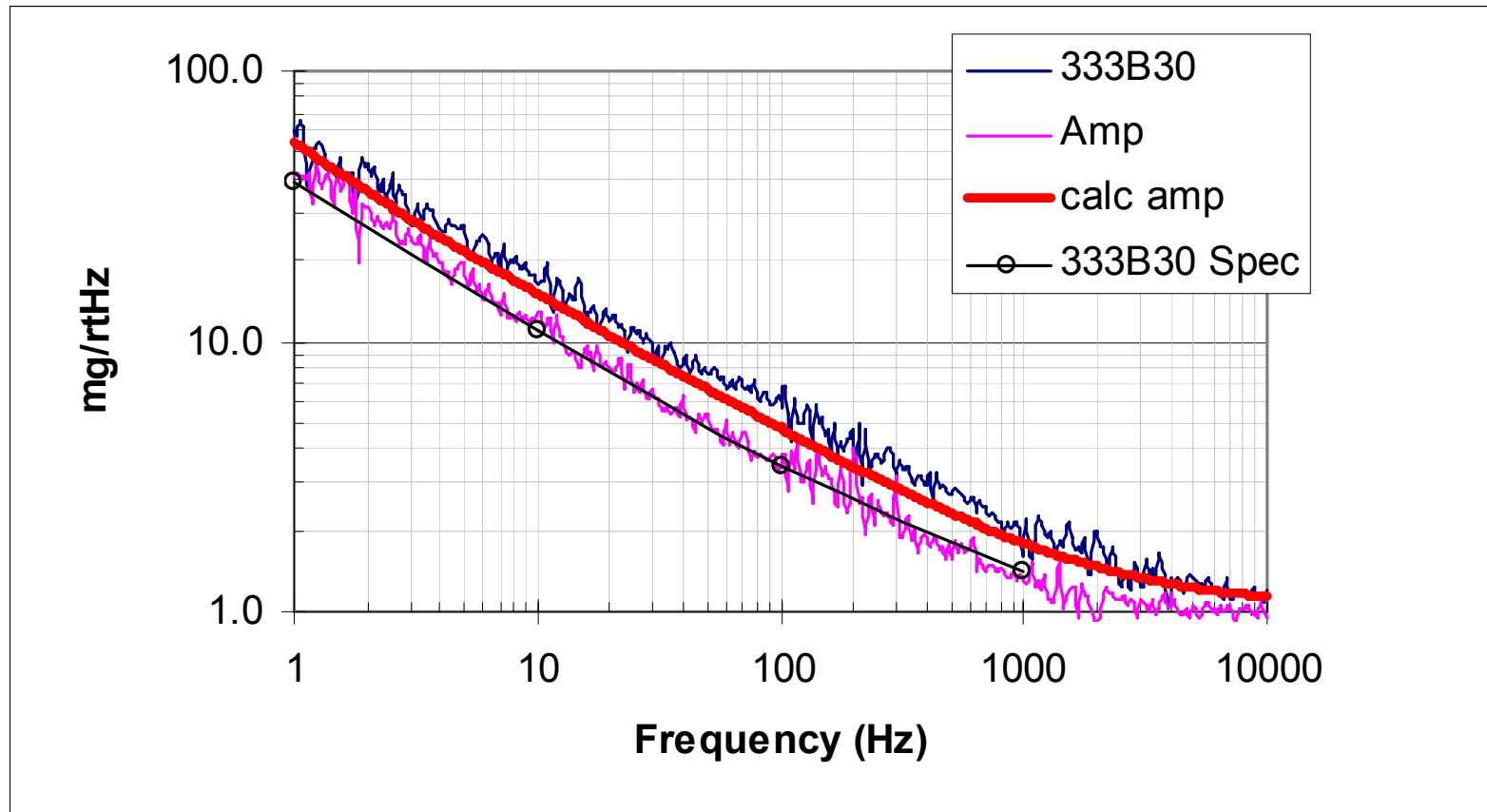- Reasonable correlation between calculation and measurement.



Design example: 333B30

- Design specs

$$C_p = 690 \text{ pF}$$

$$C_f = 50 \text{ pF}$$

$$\text{Amp Noise Gain} = (1 + 690/50) = 14.8$$


$$\text{Time constant} = 1\text{-}3 \text{ seconds}$$

$$\text{Sensitivity} = 100 \text{ mV/g}$$

- High gain and long time constant. Would expect that amplifier noise would dominate.

Design Example: 333B30

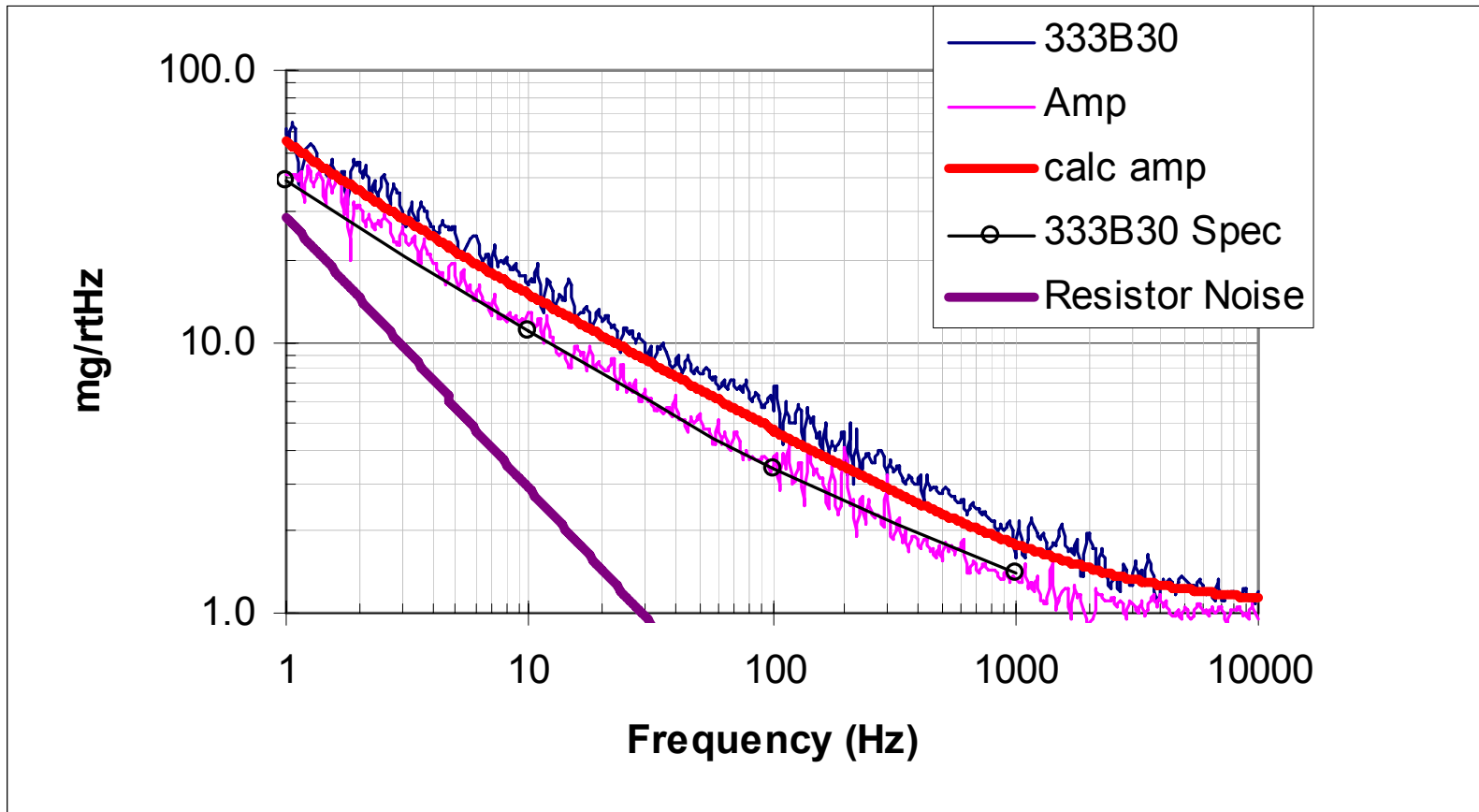- Resistor noise has no influence 1Hz to 10kHz



333B30 damping noise

- Design specs

$$Q = 50$$

$$\text{Resonance} = 44\text{kHz}$$

$$\text{Mass} = 0.7 \text{ grams}$$


- Resolution

$$\text{resolution} = \sqrt{4k_B T} \sqrt{\frac{\omega_n}{Qm}}$$

- Large Q, large mass, high frequency. Expect low damping noise floor.


333B30 Damping noise

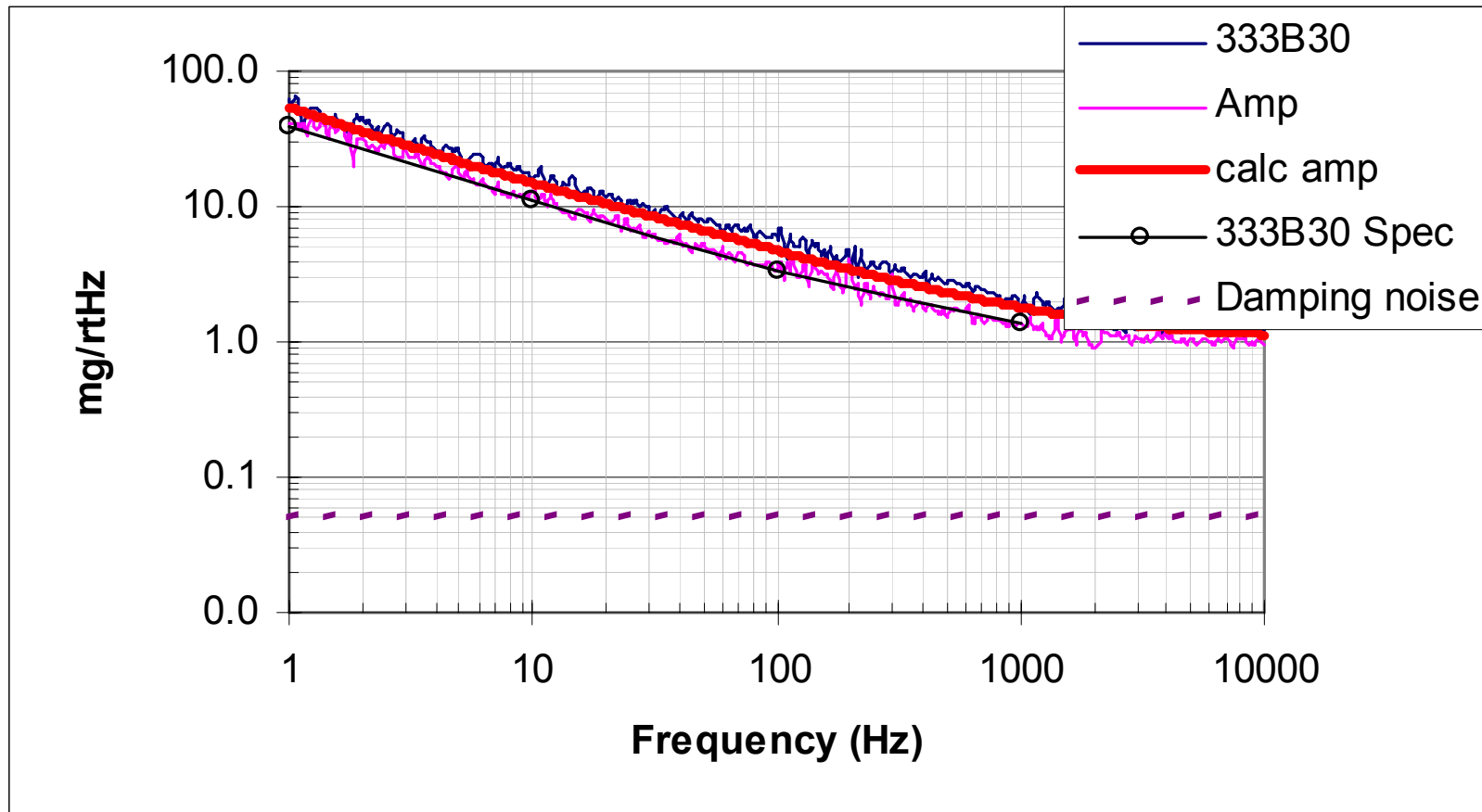- Mechanical damping does not contribute to noise.




333B30: Design trade-offs

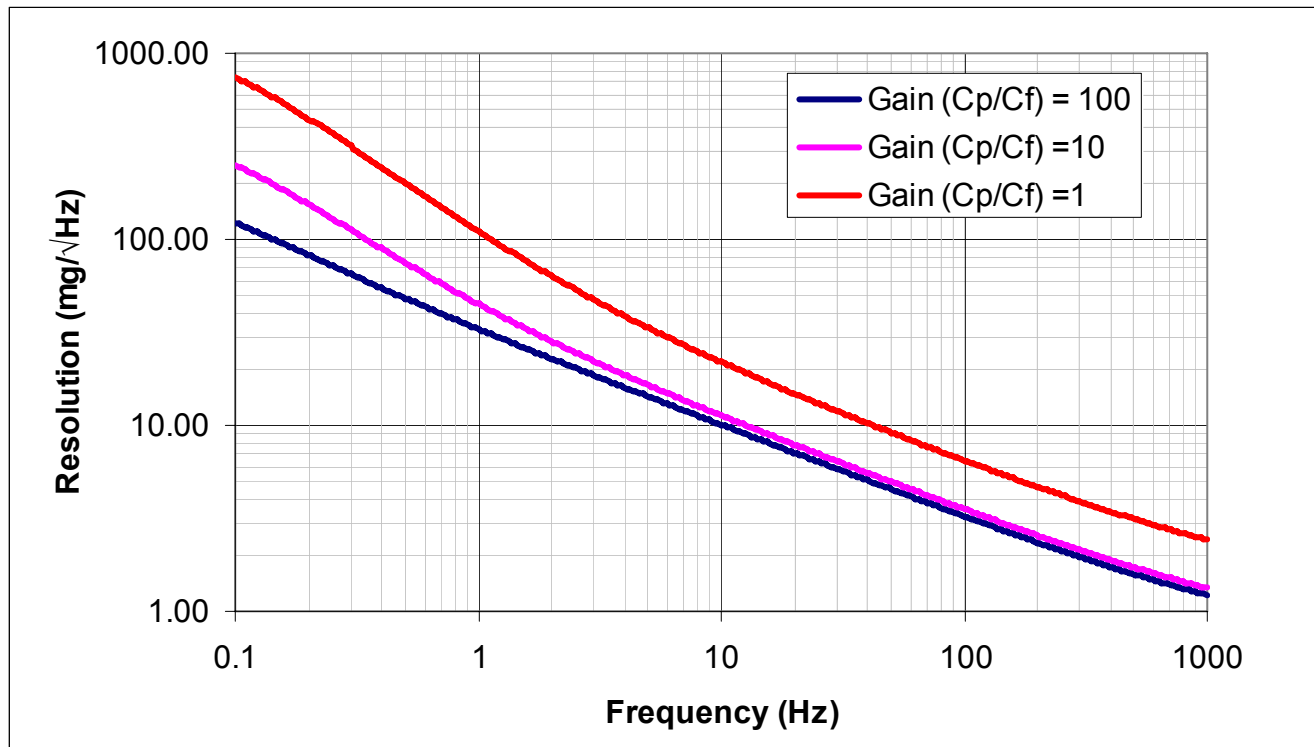- Increasing charge amp gain improves noise floor.
 - Gain multiplies signal + amp noise. No effect on R noise (100 mV/g at Gain = 100)



333B30: Design trade-offs

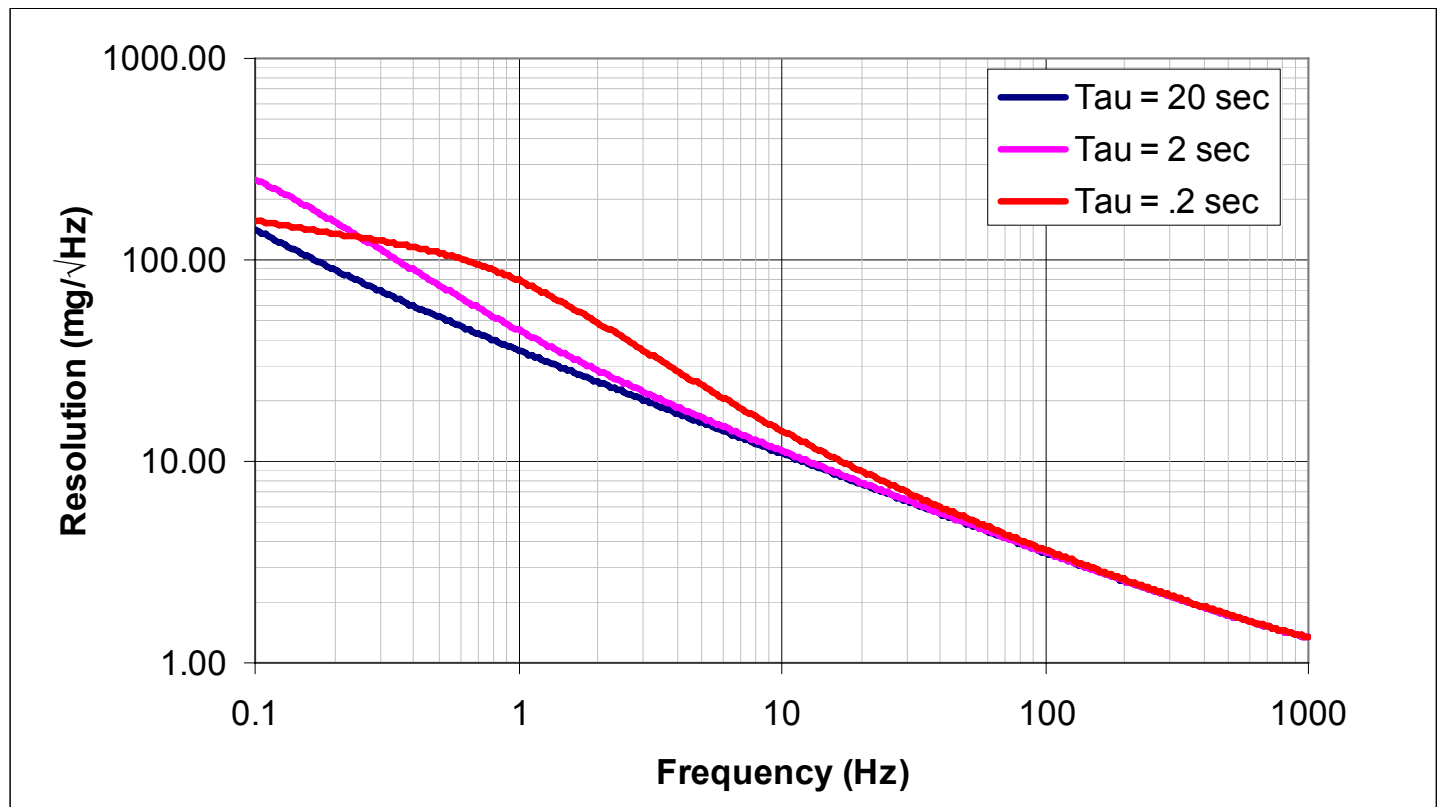- Longer time constant improves noise floor (0.5-10Hz).
 - Higher resistance, but longer time constant “pushes” noise out of band to low frequency.



Summary

- Thermal (resistor) noise dominates low frequency.
- Amp noise dominates at high frequency.
- Design trade-offs in charge amps:
 - Higher gain usually improves resolution.
 - Longer time constant usually helps low frequency resolution.



*Analysis of Electrical Noise in
Piezoelectric Sensors*

Jeffrey Dosch

Bill Hynd

PCB Piezotronics, Depew NY

IMAC XXV February 19-22, 2007

Orlando FL